# Fast bridge switching and slow three-phase voltage references

## One half bridge

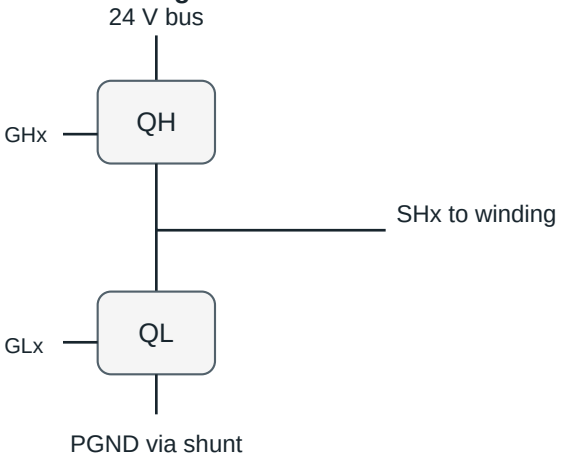


## Logic inputs to the driver

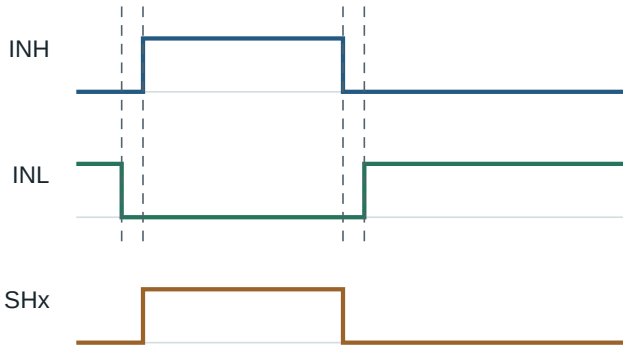


Both LOW gaps: nominal 500 ns

SHx approximately 0 or 24 V; deadtime details omitted.

## Average voltage references over one electrical turn

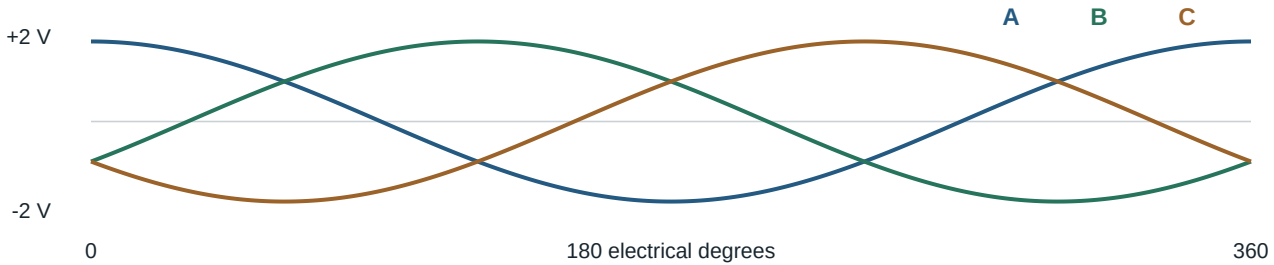


Envelopes differ by 120 electrical degrees; all PWM carriers are synchronized.